

Unit : IVElectrical CircuitsKirchhoff's law :

Kirchhoff developed two fundamental laws for analysing complicated electrical network consisting of many sources, junctions, branches. These two laws are —

- Kirchhoff's current law (KCL)
- Kirchhoff's voltage law (KVL)

1. Kirchhoff's current law (KCL) :

It states that at any instant of time algebraic sum of currents flowing to a junction point of any network is zero. That is —

$$\sum I_n = 0$$

We can easily understand from the example shown in fig 1. In fig 1, currents I_1, I_2, I_4 are taken positive and currents I_3 and I_5 are negative. Therefore, according to KCL the algebraic sum of currents are as —

$$I_1 - I_2 + I_3 + I_4 - I_5 = 0$$

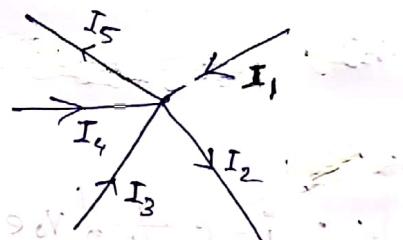


fig:1 (KCL)

2. Kirchhoff's voltage law :

It states that at any instant of time the algebraic sum of the voltage drops around a closed path in a network is zero. That is —

$$\sum V_n = 0$$

In fig 2 :-

$$IR_1 + IR_2 + IR_3 = V$$

$$\text{or } V_1 + V_2 + V_3 = V$$

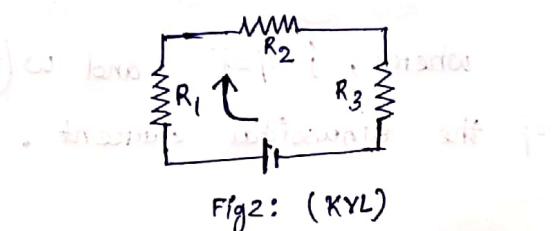


fig2: (KVL)

Reactance and impedance:

Let us consider a circuit as shown in fig.3. The instantaneous current through the capacitor is i at any instant of time t .

The current i supplied by the ac source connected to a capacitor is given by —

$$i = c \frac{dv}{dt}$$

$$= c \frac{d}{dt} \{ V_0 \sin(\omega t + \phi) \}$$

Substituting the value of voltage across the capacitor, we can write,

$$\sin(\omega t + \phi) = e^{j(\omega t + \phi)} \quad [\text{In complex notation}]$$

$$\therefore i = c \frac{d}{dt} \{ V_0 e^{j(\omega t + \phi)} \}$$

$$i = j\omega c V_0 e^{j(\omega t + \phi)}$$


Comparing eqn ① and ② we get — $j\omega c$ plays the role of R

in this circuit and current leads the voltage by an angle ϕ .

The reactance of a capacitor C in an ac circuit is defined as —

$$Z_C = 1/j\omega C \quad \rightarrow ③$$

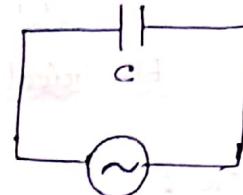where, $j = \sqrt{-1}$ and $\omega (= 2\pi f)$ is the angular frequency of the sinusoidal current.



$$V(t) = V_0 \sin(\omega t + \phi)$$

fig:3 AC supply connected to capacitor.

— and AC circuit — Redundant

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

(LX) coil transverse effect of

(LX) coil sector effect of

Similarly, let us consider the circuit in fig:4. If the current through the inductor be —

$$i(t) = I_0 e^{j(\omega t + \phi)}$$

Now,

$$\text{Voltage, } V(t) = L \frac{di}{dt}$$

$$= L \frac{d}{dt} \left\{ I_0 e^{j(\omega t + \phi)} \right\} = I_0 j\omega L e^{j(\omega t + \phi)}$$

$$\text{shift to } \Rightarrow = j\omega L I_0 e^{j(\omega t + \phi)}$$

Here, $j\omega L$ plays the same role as R and the voltage leads the current by an angle ϕ .

The reactance of an inductance L in an ac circuit is defined as —

$$Z_L = j\omega L \quad \rightarrow ⑤$$

Again,

let us consider the current $i(t)$ through a circuit be

represented as $I_0 e^{j\omega t}$. The

voltage applied to the circuit

is given as —

$$V(t) = L \frac{di}{dt} + Ri$$

$$= j\omega L I_0 e^{j\omega t} + R I_0 e^{j\omega t} \quad \rightarrow ⑥$$

$$\text{let, } R = Z \cos \phi \quad \rightarrow 6(A)$$

$$\text{and, } j\omega L = Z \sin \phi \quad \rightarrow 6(B)$$

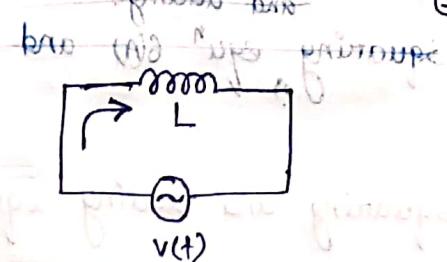


fig:4 : AC supply connected to an inductor

AC supply

connected to an inductor

Squaring and adding equation 6(A) and 6(B) we get —

$$R^2 + (j\omega L)^2 = Z^2 \cos^2 \phi + Z^2 \sin^2 \phi \quad (\text{as } \sin^2 \phi + \cos^2 \phi = 1)$$

$$\Rightarrow Z^2 = R^2 + \omega^2 L^2$$

$$\left[\begin{array}{l} \therefore \cos^2 \phi + \sin^2 \phi = 1 \\ \frac{R^2 + \omega^2 L^2}{Z^2} = 1 \Rightarrow j = \sqrt{-1} \\ j^2 = -1 \end{array} \right]$$

$$\Rightarrow Z = \sqrt{R^2 + \omega^2 L^2} \rightarrow (7)$$

and $Z = \sqrt{R^2 + \omega^2 L^2}$ is called the impedance of this circuit (fig:5).

Now,

$$\frac{6(B)}{6(A)} \Rightarrow \frac{Z \sin \phi}{Z \cos \phi} = \frac{j\omega L}{R}$$

$$\Rightarrow \tan \phi = \frac{j\omega L}{R}$$

$$\Rightarrow \phi = \tan^{-1} \frac{j\omega L}{R}$$

Now, the average power in this circuit is given by —

$$\overline{P(t)} = \overline{V(t) I(t)}$$

$$= \frac{1}{T} \int_0^T V_o I_o Z e^{j(2\omega t + \phi)} dt$$

$$= \frac{V_o I_o}{2} \cos \phi$$

$$= V_{rms} I_{rms} \cos \phi$$

From equⁿ (8), Here, $\cos \phi$ is called the power factor.

Series Resonant circuit:

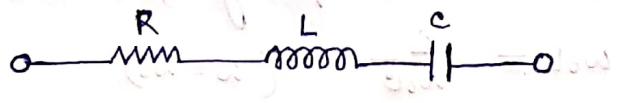


Fig.6 Series LCR circuit.

Let us consider a circuit where resistor (R), inductor (L) and capacitor (C) are connected in series as shown in the fig.6. The series R, L, C circuit shows resonance at some frequency f_0 . So this circuit is called series resonant circuit.

From the above fig.6, the total impedance of the series RLC is -

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$\text{and } \phi = \tan^{-1} \left[\frac{\left(\omega L - \frac{1}{\omega C}\right)}{R} \right]$$



Thus, the current :

through the circuit I varies with frequency of the ac sinusoidal voltage. For a given value of the peak value of sinusoidal voltage, the variation of the peak current (I) with frequency ω will be

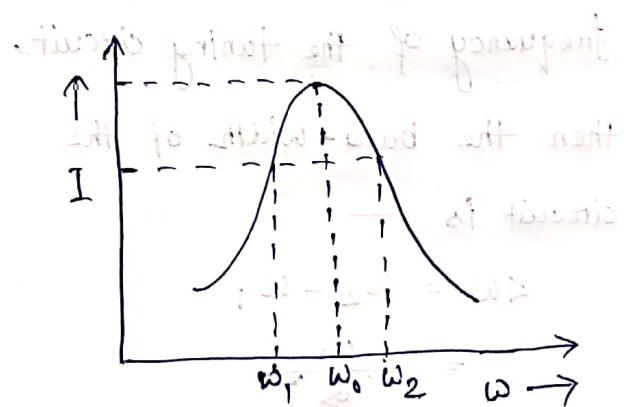


Fig.7 Frequency response of series resonant circuit.

has been shown in fig 8. The current through the circuit will be maximum at a frequency f_0 , when

$$\omega_0 L = \frac{1}{\omega_0 C} \quad (\omega = \omega_0)$$

i.e. when $|Z| = R$, the minimum possible magnitude of impedance. So at frequency f_0 [$= 1/2\pi\sqrt{LC}$] the impedance of series R, L, C circuit is minimum, and the current through the circuit is maximum. This phenomenon is called resonance.

The Q-factor of a series resonant is defined as the voltage across the inductance to the voltage across the resistance at resonance. So,

$$Q = \frac{V_L}{V_R} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R}$$

Large the Q-value more is the response of the circuit.

Now, if ω_1 and ω_2 are lower and upper half-power frequency of the tuning circuit, then the band-width of the circuit is

$$\Delta\omega = \omega_2 - \omega_1$$

$$\frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{Q}$$

$$\text{or } Q = \frac{\omega_0}{\Delta\omega}$$

So, for lower bandwidth, the Q-value of the circuit is high.

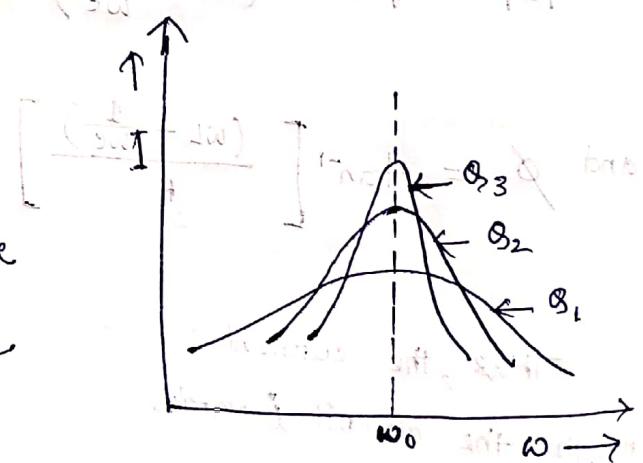


Fig:8 Frequency response of different series resonant circuits with different Q-factors.